

TGGENCO ASSISTANT ENGINEERS AND CHEMISTS RECRUITMENT EXAMINATION 14 July 2024

| | |
|--------------------|--------------------------------------|
| Hall Ticket Number | 2432990122 |
| Candidate Name | HEMANT KATTA |
| Test Center Name | Vidya Jyothi Institute of Technology |
| Test Date | 14/07/2024 |
| Test Time | 5:00 PM - 6:40 PM |
| Subject | Assistant Engineer Electronics |

Section : Section A

Q.1 Consider the self-bias circuit where $V_{CC} = 12\text{ V}$, $R_C = 5\text{ k}\Omega$, $R_E = 1\text{ k}\Omega$, $R_2 = 10\text{ K}\Omega$, $R_1 = 90\text{ k}\Omega$ and $h_{fe} = 99$. Find its stability factor

- Ans ☒ 1. 9.17
☒ 2. 16.32
☒ 3. 100
☒ 4. 10.01

Question ID : 170527522
Chosen Option : 3

Q.2 An n-bit binary counter consist of _____ flip-flops, and can count in binary from 0 to _____

- Ans ☒ 1. $n-1, 2^n$
☒ 2. $n, 2^n$
☒ 3. $n, 2^n - 1$
☒ 4. $n-1, 2^n - 1$

Question ID : 170527537
Chosen Option : 3

Q.3 A superheterodyne receiver with an IF of 450 kHz is tuned to a signal at 1200 kHz. The image frequency is

- Ans ☒ 1. 2850 kHz
☒ 2. 2100 kHz
☒ 3. 1650 kHz
☒ 4. 900 kHz

Question ID : 170527554
Chosen Option : 3

Q.4 Consider a transmission line of characteristic impedance 50Ω . Let it be terminated at one end by $+j50\text{ ohm}$. The VSWR produced by it in the transmission line will be

- Ans ☒ 1. ∞
☒ 2. $+j$
☒ 3. 0
☒ 4. $+1$

Question ID : 170527562
Chosen Option : 2

Q.5 The value of feedback resistance for an op-amp with a gain of -10 and input resistance equal to $10\text{ k}\Omega$ is

- Ans ☒ 1. $100\text{ k}\Omega$
☐ 2. $90\text{ k}\Omega$
☐ 3. $1\text{ k}\Omega$
☐ 4. $10\text{ k}\Omega$

Question ID : 170527527
Chosen Option : 4

Q.6 Convert the given expression in standard POS form

$$Y = A \cdot (A + B + C)$$

- Ans ☐ 1. $(A + B + C)(A + \bar{B} + C)(A + B + \bar{C})$
☒ 2. $(A + B + C)(A + \bar{B} + C)(A + B + \bar{C})(A + \bar{B} + \bar{C})$
☐ 3. $(A + B \cdot \bar{B} + C\bar{C})(A + B + C)$
☐ 4. $(A + B + C)(\bar{A} + \bar{B} + C)(\bar{A} + B + \bar{C})(A + \bar{B} + \bar{C})$

Question ID : 170527532
Chosen Option : 1

Q.7 As electromagnetic waves travel in free space, only one of the following can happen to them.

- Ans ☐ 1. Absorption
☐ 2. Refraction
☒ 3. Attenuation
☐ 4. Reflection

Question ID : 170527560
Chosen Option : 1

Q.8 For a closed-loop system with loop transfer function $L(s)$ is of _____ type, the system is _____ if the $L(s)$ plot that corresponds to the Nyquist path does not enclose the $(-1, j0)$ point.

- Ans ☐ 1. Maximum-phase, unstable
☐ 2. Maximum-phase, stable
☐ 3. Minimum-phase, unstable
☒ 4. Minimum-phase, stable

Question ID : 170527544
Chosen Option : 2

Q.9 The equation for frequency of oscillations of Wein Bridge oscillator using op-amp is

Ans

- ☒ 1. $\frac{1}{2\pi RC\sqrt{6}}$
- ☒ 2. $2\pi RC$
- ☒ 3. $\frac{1}{\sqrt{2\pi RC}}$
- ☒ 4. $\frac{1}{2\pi RC}$

Question ID : 170527529
Chosen Option : 3

Q.10 A quantum dot is an example of

Ans

- ☒ 1. 3 – D Nano structure
- ☒ 2. 1 – D Nano structure
- ☒ 3. 2 – D Nano structure
- ☒ 4. Zero – Dimensional Nano structure

Question ID : 170527567
Chosen Option : 4

Q.11 Which one is correct with respect to a simple AGC in a radio receiver?

Ans

- ☒ 1. The audio stage gain is normally controlled by the AGC
- ☒ 2. The faster the AGC time constant the more accurate the output
- ☒ 3. An increase in signal strength produces more AGC
- ☒ 4. The highest AGC voltage is produced

Question ID : 170527553
Chosen Option : 2

Q.12 The Avalanche breakdown occurs in lightly doped diodes where the depletion layer is _____ and electric field is _____

Ans

- ☒ 1. Very low, very high
- ☒ 2. Very low, very low
- ☒ 3. Very wide, very low
- ☒ 4. Very wide, very high

Question ID : 170527514
Chosen Option : 1

Q.13 Which one of the following statement is false?

Ans ☒ 1.

Conductors are formed using metallic bonding and has positive temperature coefficient

☒ 2.

Insulators are formed due to ionic bonding and has negative temperature coefficient

☒ 3.

Semiconductors are formed due to metallic bonding and has low resistance

☒ 4.

Semiconductors are formed due to covalent bonding and has negative temperature coefficient

Question ID : 170527511

Chosen Option : 4

Q.14 The standard reference antenna for the directive gain is

Ans ☒ 1. Isotropic antenna

☒ 2. Infinitesimal dipole

☒ 3. Half-wave dipole

☒ 4. Elementary doublet

Question ID : 170527563

Chosen Option : 3

Q.15 Laser diode has a threshold level of current, above which the laser action occurs and below which the laser diode behaves like a

Ans ☒ 1. LCD emitting coherent light

☒ 2. LED emitting incoherent light

☒ 3. PN junction diode

☒ 4. Highly doped Zener diode

Question ID : 170527515

Chosen Option : 2

Q.16 A Ge (Germanium) diode has a saturation current of $10\ \mu\text{A}$ at 27°C . Find the saturation current at 127°C ?

Ans ☒ 1. $1.27\ \text{mA}$

☒ 2. $10.24\ \text{mA}$

☒ 3. $20\ \mu\text{A}$

☒ 4. $10\ \mu\text{A}$

Question ID : 170527517

Chosen Option : 1

Q.17 How can a D flip-flop be converted into a T flip-flop?

Ans ☒ 1. $D = T \oplus \bar{Q}$

☒ 2. $D = T \oplus Q$

☒ 3. $D = T\bar{Q}$

☒ 4. $D = TQ$

Question ID : 170527536

Chosen Option : 1

Q.18 Which of the following powerplants results into comparatively less carbon foot print?

- Ans ☒ 1. Diesel power plant
☒ 2. Hydroelectric plant
☒ 3. Gas Turbine plant
☒ 4. Steam power plant

Question ID : 170527572
 Chosen Option : 1

Q.19 For a dual slope ADC type $3\frac{1}{2}$ digit DVM, the reference voltage is 100 mV and the first integration time is set to 300 ms. For some input voltage, the “disintegration” period is 370.2 ms. The DVM will indicate _____

- Ans ☒ 1. 100.0 mV
☒ 2. 1.414 V
☒ 3. 199.9 mV
☒ 4. 123.4 mV

Question ID : 170527538
 Chosen Option : 1

Q.20 A hydroelectric power plant generates

- Ans ☒ 1. Solar energy from the water reflection currents
☒ 2. Electrical energy from the stored temperature of water
☒ 3. Electrical energy from the moving water currents
☒ 4. Chemical energy from the stagnant water currents

Question ID : 170527570
 Chosen Option : 3

Q.21 The modulation index of an Amplitude Modulated wave is changed from 0 to 1. The transmitted power is

- Ans ☒ 1. Increased by 50 percent
☒ 2. Decreased by 75 percent
☒ 3. Decreased by 50 percent
☒ 4. Increased by 75 percent

Question ID : 170527551
 Chosen Option : 1

Q.22 Given the autocorrelation function for a stationary process is $R_{XX}(\tau) = 25 + \frac{4}{1+6\tau}$.

Find the variance of the process X(t)

- Ans ☒ 1. 14.28
☒ 2. 25
☒ 3. 4
☒ 4. 29


Question ID : 170527547
 Chosen Option : 4

Q.23 In free space $\vec{E}(z, t) = 50 \cos(\omega t - \beta z) \vec{a}_x$ (V/m), then average power crossing a circular area of radius 2.5 m in the plane $z = \text{constant}$ is

- Ans ☒ 1. 64.2 W
☒ 2. 32.5 W
☒ 3. 130.2 W
☒ 4. 65.1 W

Question ID : 170527561
 Chosen Option : 4

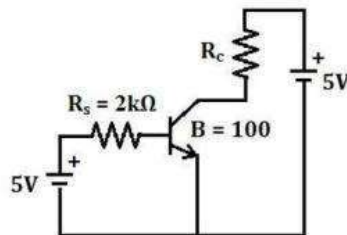Q.24 The transistor in the given circuit should always be in the active region. Take $V_{CE(\text{sat})} = 0.2\text{V}$, $V_{BE} = 0.7\text{V}$. The range of R_C in Ω , which can be used is



- Ans ☒ 1. $28 < R_C < 29$
☒ 2. $19 < R_C < 21$
☒ 3. $22 < R_C < 23$
☒ 4. $30 < R_C < 32$


Question ID : 170527523
 Chosen Option : 3

Q.25 For the equation $\ddot{x}(t) + 3\dot{x}(t) + 2x(t) = 5$, the solution $x(t)$ approaches which of the following values as $t \rightarrow \infty$?

- Ans ☒ 1. 0
☒ 2. 10
☒ 3. $\frac{5}{2}$
☒ 4. 5

Question ID : 170527507
 Chosen Option : 3

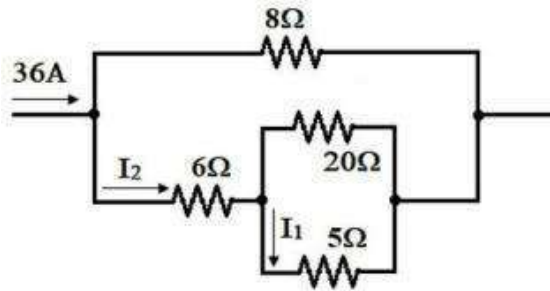Q.26 Find current I_1 in the following circuit



- Ans
- ☒ 1. 2 A
 - ☒ 2. 4.2 A
 - ☒ 3. 12.8 A
 - ☒ 4. 16 A

Question ID : 170527501
Chosen Option : 1

Q.27 In which of the following modulation technique, two or more bits are made for transmitting at once on a single signal?

- Ans
- ☒ 1. ASK
 - ☒ 2. PSK
 - ☒ 3. M-ary ASK
 - ☒ 4. FSK

Question ID : 170527556
Chosen Option : 3

Q.28 Match the following:

| | | | |
|-----|-------------|-------|---|
| (a) | Linear | (i) | $y(n) = \sum_{k=-\infty}^{\infty} x(k)$ |
| (b) | Non- linear | (ii) | $y(n) = x^2(n)$ |
| (c) | Causal | (iii) | $y(n) = x(-n)$ |
| (d) | Non-causal | (iv) | $y(n) = x(n^2)$ |

- Ans
- ☒ 1. a – iv, b- ii , c- i, d-iii
 - ☒ 2. a – i, b- ii , c- iii, d-iv
 - ☒ 3. a – iv, b- i , c-ii, d-iii
 - ☒ 4. a – ii, b-i, c-iii, d-iv

Question ID : 170527510
Chosen Option : 3

Q.29 The hole concentration in p-type GaAs is given by $P = 10^{16} \left(1 - \frac{x}{L}\right) \text{ cm}^{-3}$ for $0 \leq x \leq L$ where $L = 10 \mu\text{m}$. If hole diffusion coefficient is $10 \text{ cm}^2/\text{s}$ then hole diffusion current density at $x = 5 \mu\text{m}$ is

- Ans
- ☒ 1. 16 A/cm²
 - ☒ 2. 20 A/cm²
 - ☒ 3. 30 A/cm²
 - ☒ 4. 24 A/cm²

Question ID : 170527513
Chosen Option : 2

Q.30 The Hot wire anemometers are used to measure

- Ans
- ☐ 1. Temperature
 - ☐ 2. Humidity
 - ☐ 3. Weight
 - ☒ 4. Fluid flow

Question ID : 170527580
Chosen Option : 4

Q.31 A Wheatstone bridge requires a change of $7\ \Omega$ in the unknown arm of the bridge to produce a change in deflection of 3 mm of the galvanometer. Determine the sensitivity.

- Ans
- ☐ 1. $2.67\ \Omega/\text{mm}$
 - ☐ 2. $1.15\ \Omega/\text{mm}$
 - ☐ 3. $21\ \text{mm}.\Omega$
 - ☒ 4. $0.429\ \text{mm}/\Omega$

Question ID : 170527574
Chosen Option : 2

Q.32 Match the following:

| | | | |
|-----|--------------|-------|----------------------------------|
| (a) | Pitot tube | (i) | velocity to pressure |
| (b) | Hydrometer | (ii) | Temperature to electric current |
| (c) | Thermocouple | (iii) | pressure to displacement |
| (d) | Bourdon tube | (iv) | specific gravity to displacement |

- Ans
- ☐ 1. a – iii, b – ii, c – i, d – iv
 - ☐ 2. a – iv, b – i, c – iii, d – ii
 - ☒ 3. a – i, b – iv, c – ii, d – iii
 - ☐ 4. a – ii, b – iii, c – iv, d – i

Question ID : 170527579
Chosen Option : 2

Q.33 $y(n) = x(n) - 2x(n-1) + x(n-2)$ is a good approximation to

- Ans
- ☐ 1. BSF passing $\frac{\pi}{8} \leq |w| \leq \frac{\pi}{4}$
 - ☐ 2. LPF
 - ☒ 3. HPF
 - ☐ 4. BPF passing $\frac{\pi}{8} \leq |w| \leq \frac{\pi}{4}$

Question ID : 170527508
Chosen Option : 4


Q.34 A wide-band pass active filter having a gain of 4, $f_l = 20$ Hz and $f_h = 2$ KHz. Find the value of Q of the filter?

- Ans
- ☒ 1. 0.0001
 - ☒ 2. 0.0101
 - ☒ 3. 0.1010
 - ☒ 4. 10000

Question ID : 170527530

Chosen Option : 3

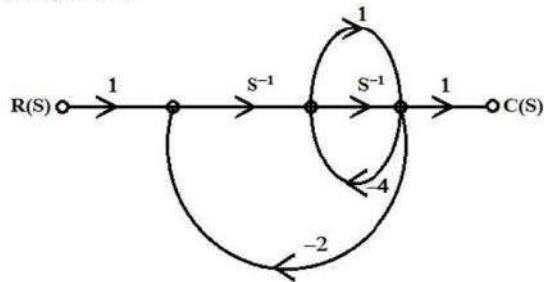Q.35 The signal flow graph of a system is shown in figure. The transfer function $\frac{C(s)}{R(s)}$ of the system is



- Ans
- ☒ 1. $\frac{S(S+2)}{S^2 + 29S + 6}$
 - ☒ 2. $\frac{6S}{S^2 + 29S + 6}$
 - ☒ 3. $\frac{(S+1)}{5S^2 + 6S + 2}$
 - ☒ 4. $\frac{6}{S^2 + 29S + 6}$

Question ID : 170527545

Chosen Option : 4


Q.36 What is the unit of permeability in magnetic materials?

- Ans
- ☒ 1. Weber/m
 - ☒ 2. Ampere-turns/weber
 - ☒ 3. Henry/m
 - ☒ 4. Ampere-turns/m

Question ID : 170527568

Chosen Option : 1

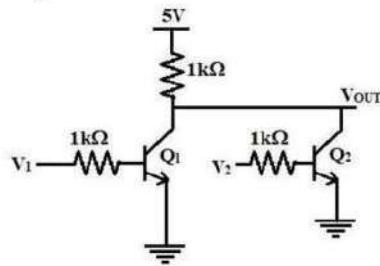
Q.37 Which of the following logical gate is implemented using the circuit shown below where V_1 and V_2 are inputs (with 0 V as digital 0 and 5 V as digital 1) and V_{OUT} is the output?



- Ans ☒ 1. XOR
☒ 2. NOR
☒ 3. NOT
☒ 4. NAND

Question ID : 170527531
 Chosen Option : 1

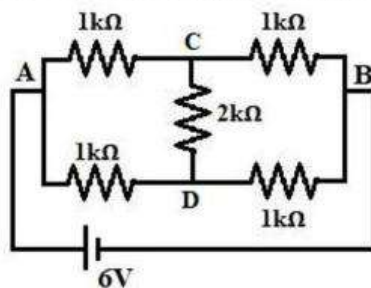Q.38 The current through the $2k\Omega$ resistance in the circuit shown in figure is



- Ans ☒ 1. 1 mA
☒ 2. 3 mA
☒ 3. 6 mA
☒ 4. 0 mA

Question ID : 170527504
 Chosen Option : 1

Q.39 A $10\text{ k}\Omega$ variable resistance has a linearity of 0.1% and the movement of contact is 320° . If the instrument is to be used as a potentiometer with a linear scale of 0 to 1.6 V. Determine the maximum voltage error.

- Ans ☒ 1. 1.0 V
☒ 2. 1.6 mV
☒ 3. 3.2 V
☒ 4. 0.1 mV

Question ID : 170527575
 Chosen Option : 2

Q.40 Consider a characteristic equation given by $S^4 + 3S^3 + 5S^2 + 6S + k + 10 = 0$. The condition for stability is

- Ans
- ☒ 1. $-10 < k$
 - ☒ 2. $k > -4$
 - ☒ 3. $k > 5$
 - ☒ 4. $-10 < k < -4$

Question ID : 170527546
Chosen Option : 4

Q.41 The power spectrum $S_{XX}(w)$ for the random process that has the autocorrelation function of $R_{XX}(\tau) = (A^2/2)\cos(w_0\tau)$ is

- Ans
- ☒ 1. $2\pi\delta(w + w_0)$
 - ☒ 2. $\frac{A^2\pi}{2}[\delta(w - w_0) - \delta(w + w_0)]$
 - ☒ 3. $\frac{A^2\pi}{2}[\delta(w - w_0) + \delta(w + w_0)]$
 - ☒ 4. $2\pi\delta(w - w_0)$

Question ID : 170527548
Chosen Option : 3

Q.42 Identify the wrong answer with the properties of ceramics.

- Ans
- ☒ 1. Good thermal insulator
 - ☒ 2. Low tensile strength
 - ☒ 3. High hardness
 - ☒ 4. High mass density

Question ID : 170527569
Chosen Option : 3

Q.43 The dc load line on the output characteristics of a transistor gives the following information except

- Ans
- ☒ 1. Thermal runaway
 - ☒ 2. Active region
 - ☒ 3. Cutoff point
 - ☒ 4. Saturation point

Question ID : 170527519
Chosen Option : 2

Q.44 The Power density of white noise is
(η is a real positive constant)

- Ans
- ☒ 1. $\frac{\eta}{2}$
 - ☐ 2. 2η
 - ☐ 3. η
 - ☐ 4. η^2

Question ID : 170527549
Chosen Option : 1

Q.45 The motion of charge carrier from region of higher concentration to lower concentration leads to a current called

- Ans
- ☐ 1. Cut off current
 - ☐ 2. Drift current
 - ☐ 3. Pinch off current
 - ☒ 4. Diffusion current

Question ID : 170527512
Chosen Option : 2

Q.46 Which of the following is used to reduce the number of data lines required for transmission of occurrences of events?

- Ans
- ☐ 1. Adder
 - ☐ 2. Seven segment decoder
 - ☐ 3. Decoder
 - ☒ 4. Encoder

Question ID : 170527533
Chosen Option : 4

Q.47 The complex frequency $s = \sigma + jw$ is the general case; then which of the following is correct?

- Ans
- ☐ 1. $s = \infty \rightarrow \text{sinusoidal}; w = \infty \rightarrow \text{exponential}; \sigma = 0 \rightarrow dc$
 - ☐ 2. $s = 0 \rightarrow \text{exponential}, w = \infty \rightarrow \text{sinusoidal}; \sigma = 0 \rightarrow dc$
 - ☒ 3. $s = 0 \rightarrow dc, w = 0 \rightarrow \text{exponential}; \sigma = 0 \rightarrow \text{sinusoidal}$
 - ☐ 4. $s = \infty \rightarrow \text{exponential}; w = 0 \rightarrow dc; \sigma = \infty \rightarrow \text{sinusoidal}$

Question ID : 170527506
Chosen Option : 2

Q.48 The ratio of current of injected carriers into the base to the total emitter current is called

- Ans ☒ 1. DC current gain
☒ 2. Emitter efficiency
☒ 3. Base transport factor
☒ 4. Large signal current gain

Question ID : 170527518
 Chosen Option : 2

Q.49 Consider a linear DM system designed to accommodate analog message signals limited to bandwidth of 3.5 kHz. A sinusoidal test signals of amplitude $A_{\max} = 1\text{ V}$ and frequency $f_m = 800\text{ Hz}$ is applied to the system. The sampling rate of the system is 64kHz. Minimum value of the step size to avoid overload is

- Ans ☒ 1. 240 mV
☒ 2. 120 mV
☒ 3. 78.5 mV
☒ 4. 67.25 mV

Question ID : 170527557
 Chosen Option : 3

Q.50 Power consumed by a balanced 3-phase, 3-wire load is measured by the two wattmeter method. The first wattmeter reads twice that of the second. Then the load impedance angle in radians is

- Ans ☒ 1. $\pi/3$
☒ 2. $\pi/6$
☒ 3. $\pi/2$
☒ 4. $\pi/8$

Question ID : 170527576
 Chosen Option : 2

Q.51 Match the following with respect to the characteristics of actual signals which severely strain a control system and their models

| | | | |
|-----|--------------------------|-------|--------------------|
| (a) | sudden shock | (i) | ramp function |
| (b) | sudden change | (ii) | parabolic function |
| (c) | linear change with time | (iii) | impulse function |
| (d) | faster changes with time | (iv) | step function |

- Ans ☒ 1. a – iv, b – i, c – iii, d – ii
☒ 2. a – ii, b – i, c – iv, d – iii
☒ 3. a – iii, b – iv, c – i, d – ii
☒ 4. a – i, b – ii, c – iv, d – iii

Question ID : 170527542
 Chosen Option : 3

Q.52 An industrial consumer has a daily load pattern of 2000 kW, 0.8 lag for 12 hours and 1000 kW unity power factor for 12 hours. The load factor is

- Ans ☒ 1. 0.75
☐ 2. 0.6
☐ 3. 2.0
☐ 4. 0.5

Question ID : 170527571
Chosen Option : 2

Q.53 The unilateral z-transform is restricted only to the analysis of

- Ans ☒ 1. Causal systems with causal inputs
☐ 2. Causal systems with non-causal inputs
☐ 3. Non-causal systems with non-causal inputs
☐ 4. Non-causal systems with causal inputs

Question ID : 170527509
Chosen Option : 4

Q.54 How can a decoder be converted into a demultiplexer?

- Ans ☐ 1. By adding subtractor
☐ 2. With Ex-OR gate
☐ 3. By adding one inverter
☒ 4. With enable input

Question ID : 170527534
Chosen Option : 3

Q.55 Good voice reproduction via PCM requires 128 quantization levels. Its bandwidth of voice channel is 4kHz, then data rate is

- Ans ☐ 1. 256 kbps
☐ 2. 28 kbps
☒ 3. 56 kbps
☐ 4. 128 kbps

Question ID : 170527555
Chosen Option : 4

Q.56 The bandwidth required for transmitting binary FSK signal is

- Ans ☐ 1. $2 f_b$
☐ 2. $f_b/2$
☒ 3. $4 f_b$
☐ 4. f_b

Question ID : 170527558
Chosen Option : 4

Q.57 When identical amplifier stages are cascaded, then the overall value of

Ans ☒ 1. bandwidth is higher than of an individual stage

☒ 2.

higher cut off frequency is higher than of an individual stage

☒ 3.

lower cut off frequency is higher than of an individual stage


☒ 4.

lower cut off frequency is lower than of an individual stage

Question ID : 170527524

Chosen Option : 1

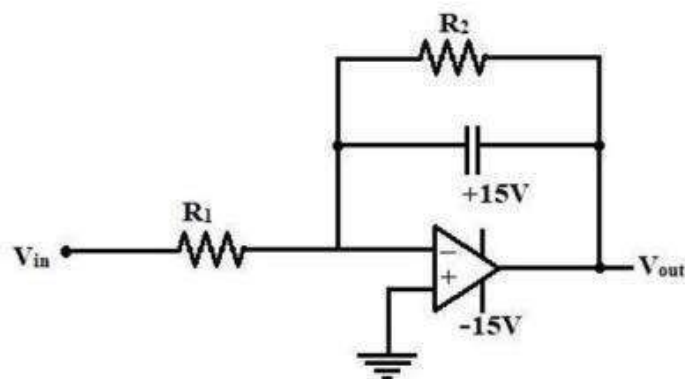Q.58 The circuit shown below is an example of a



Ans ☒ 1. High pass filter

☒ 2. Band pass filter


☒ 3. Notch filter

☒ 4. Low pass filter

Question ID : 170527528

Chosen Option : 2

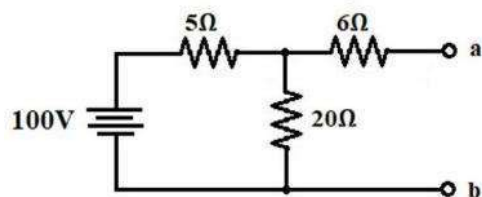Q.59 Identify the resistor that draws a current of 5A when connected across terminals 'a' and 'b' of the circuit shown in figure below?



Ans ☒ 1. 20 Ω

☒ 2. 6 Ω

☒ 3. 5 Ω

☒ 4. 4 Ω

Question ID : 170527502

Chosen Option : 1

Q.60 The simultaneous application of signals $x(t)$ and $y(t)$ to the horizontal and vertical plates, respectively of an oscilloscope, produces a vertical figure of 8 display. If P and Q are equal and $x(t) = P \sin(4t)$ then $y(t)$ is equal to

- Ans
- ☐ 1. $Q \sin(6t)$
 - ☐ 2. $Q \sin(4t)$
 - ☒ 3. $Q \sin(2t)$
 - ☐ 4. $Q \sin(8t)$

Question ID : 170527577
Chosen Option : 2

Q.61 Which of the following motor produces constant speed throughout the process?

- Ans
- ☐ 1. Stepper motor
 - ☒ 2. Synchronous motor
 - ☐ 3. DC series motor
 - ☐ 4. Universal motor

Question ID : 170527566
Chosen Option : 2

Q.62 The instrument used to measure relative amplitudes of single frequency components in a complex waveform is

- Ans
- ☐ 1. CRO
 - ☒ 2. Wave analyzer
 - ☐ 3. Instrumentation amplifier
 - ☐ 4. Ratio meter

Question ID : 170527578
Chosen Option : 1

Q.63 Find the result of the following program?

```
MOV R0, A
XOR A, #3Fh
XOR A, R0
```

- Ans
- ☒ 1. $3Fh = A \text{ XOR } N$
 - ☐ 2. $N = A \text{ XOR } 3Fh$
 - ☐ 3. $A = 3Fh \text{ XOR } N$
 - ☐ 4. $A = 3Fh \text{ XOR } A \text{ XOR } R0$

Question ID : 170527541
Chosen Option : 2

Q.64 Consider a parallel RLC circuit having an inductance of 10mH and a capacitance of 100 μ F. Determine the resistor value that would lead to overdamped response.

- Ans
- ☐ 1. $R > 5\Omega$
 - ☐ 2. $R > 10\Omega$
 - ☒ 3. $R < 5\Omega$
 - ☐ 4. $R > 100\Omega$

Question ID : 170527505
Chosen Option : 2

Q.65 The restorer is a

- Ans ☒ 1. Clamper
☒ 2. Clipper
☒ 3. Rectifier
☒ 4. Summer

Question ID : 170527525
 Chosen Option : 3

Q.66 Two 100 μ A full scale PMMC meters are employed to construct a 10 V and a 100 V full scale voltmeter. These meters will have figure of merit is

- Ans ☒ 1. 10 k Ω /V and 100 k Ω /V
☒ 2. 10 k Ω /V and 1 k Ω /V
☒ 3. 10 k Ω /V and 10 k Ω /V
☒ 4. 100 k Ω /V and 10 k Ω /V


Question ID : 170527573
 Chosen Option : 1

Q.67 In the spectrum of frequency modulated wave

- Ans ☒ 1. The total number of sidebands depends on the modulation index
☒ 2. The carrier frequency disappears when the modulation index is large
☒ 3. The amplitude of any sideband depends on the modulation index
☒ 4. The carrier frequency cannot disappear with the modulation index

Question ID : 170527552
 Chosen Option : 3

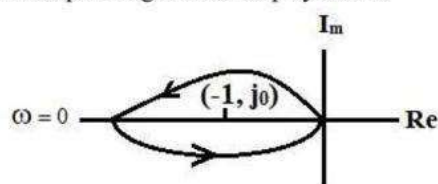Q.68 The Nyquist plot of $G(s)H(s)$, which has one right hand pole is given below. The corresponding closed loop system is



- Ans ☒ 1. stable
☒ 2. unstable with two righthand poles
☒ 3. unstable with one righthand pole
☒ 4. unstable with three righthand poles

Question ID : 170527543
 Chosen Option : 1

Q.69 Latch is a sequential circuit that takes all its inputs _____ and changes its output accordingly at any time _____ of a clock signal

- Ans
- ☒ 1. Samples, dependent
 - ☒ 2. Samples, independent
 - ☒ 3. Continuously, dependent
 - ☒ 4. Continuously, independent


Question ID : 170527539
Chosen Option : 1

Q.70 Which of the following one is not correct with respect to Faraday's law?

- Ans
- ☒ 1. The emf induced in a conductor is inversely proportional to the rate of change of flux linked with the conductor
 - ☒ 2. The value of the emf produced is directly proportional to the rate of change of flux linked with the conductor
 - ☒ 3. When a changing flux is linked with the circuit, an emf is induced in the circuit
 - ☒ 4. Whenever a conductor cuts across the magnetic lines of force, an emf is induced in it

Question ID : 170527564
Chosen Option : 2

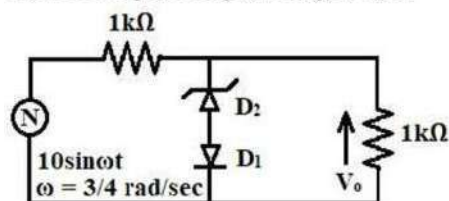Q.71 The cut in voltage of both Zener diode D_2 & pn diode D_1 shown in figure is 0.7 V, while breakdown voltage of the Zener is 3.3 V and reverse breakdown of D_1 is 50 V. The other parameters can be assumed to be the same as those of an ideal diode. The value of the peak output voltage (V_o) is



- Ans
- ☒ 1. 0.7V in the positive half cycle
 - ☒ 2. 3.3V in the positive half cycle
 - ☒ 3. 4V in the positive half cycle
 - ☒ 4. 5V in the positive half cycle

Question ID : 170527521
Chosen Option : 2

Q.72 In n-channel enhancement MOSFET, at a fixed drain voltage, the drain current is

Ans ☒ 1.

zero at zero gate voltage and it increases with the positive applied gate voltage

☒ 2.

a finite value at zero gate voltage and it increases or decreases with the applied voltage of proper polarity

☒ 3.

maximum at zero gate voltage and it decreases with applied negative gate voltage


☒ 4.

zero for negative bias voltage to gate and it increases as the negative gate bias is decreased in magnitude

Question ID : 170527516

Chosen Option : 1

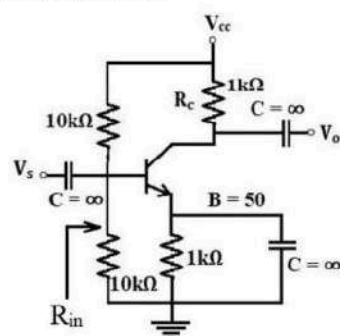Q.73 The transconductance g_m of the transistor shown in figure is 10mS . The value of input resistance R_{in} is



Ans ☒ 1. $5\text{ k}\Omega$

☒ 2. $2.5\text{ k}\Omega$

☒ 3. $8.3\text{ k}\Omega$

☒ 4. $10\text{ k}\Omega$

Question ID : 170527526

Chosen Option : 2

Q.74 Match the following:

| | | | |
|-----|--------------|-------|---------------------|
| (a) | Primary cell | (i) | fluid in paste form |
| (b) | Daniel cell | (ii) | one fluid cell |
| (c) | Dry cell | (iii) | chemical action |
| (d) | Voltaic cell | (iv) | two fluid cell |

Ans ☒ 1. a – iv, b – i, c – ii, d – iii

☒ 2. a – ii, b – iii, c – iv, d – i

☒ 3. a – iii, b – iv, c – i, d – ii

☒ 4. a – i, b – ii, c – iii, d – iv

Question ID : 170527565

Chosen Option : 2

Q.75 The cladding which surrounds the fiber core

- Ans
- ☒ 1. Ensures that the refractive index remains constant
 - ☒ 2. Acts to help guide the light in the core
 - ☐ 3. Is used to protect the fiber
 - ☐ 4. Is used to reduce optical interference

Question ID : 170527559
Chosen Option : 3

Q.76 The DRAM stores binary information in

- Ans
- ☐ 1. programmable AND array
 - ☐ 2. internal latches
 - ☐ 3. programmable OR array
 - ☒ 4. the form of electric charges on capacitors

Question ID : 170527540
Chosen Option : 4

Q.77 For a J-K flipflop, its J input is tied to its own \bar{Q} output and the K input is connected to its own Q output. If the flipflop is fed with a clock of frequency 1 MHz, its Q output frequency will be

- Ans
- ☐ 1. 5 MHz
 - ☐ 2. 1 MHz
 - ☒ 3. 0.5 MHz
 - ☐ 4. 10 MHz

Question ID : 170527535
Chosen Option : 3

Q.78 In which of the following region the FET behaves like a resistor?

- Ans
- ☒ 1. Ohmic
 - ☐ 2. Pinch off
 - ☐ 3. Saturation
 - ☐ 4. Breakdown

Question ID : 170527520
Chosen Option : 2

Q.79 If S has 3 symbols with probabilities $\frac{1}{4}$, $\frac{1}{2}$ and $\frac{1}{4}$ then the binary entropy of S is

- Ans
- ☐ 1. 1
 - ☒ 2. $\frac{3}{2}$
 - ☐ 3. $\frac{1}{2}$
 - ☐ 4. $\frac{1}{4}$

Question ID : 170527550
Chosen Option : 1

Q.80 A circuit reduced to a single equivalent capacitance C and a single equivalent resistance R will have a natural response given by $v(t) = v_0 e^{-t/\tau}$ where τ is

- Ans
- ☐ 1. $1/RC$
 - ☐ 2. C/R
 - ☐ 3. R/C
 - ☒ 4. RC

Question ID : 170527503
Chosen Option : 1

Section : Section B

Q.81 A person celebrated his birthday on 12th December 1959. If it was on a Saturday, when will he celebrate his next birthday again on Saturday?

- Ans
- ☒ 1. 12th December 1964
 - ☐ 2. 12th December 1963
 - ☐ 3. 12th December 1965
 - ☐ 4. 12th December 1966

Question ID : 170527584
Chosen Option : 2

Q.82 Fill in the blank with suitable form of the verb:
John's answers _____ his attitude.

- Ans
- ☐ 1. reflects
 - ☐ 2. are reflected
 - ☒ 3. reflect
 - ☐ 4. Have been reflected

Question ID : 170527589
Chosen Option : 3

Q.83 Which of the following is not a web browser?

- Ans
- ☐ 1. Google Chrome
 - ☐ 2. Internet Explorer
 - ☐ 3. Firefox
 - ☒ 4. Ubuntu

Question ID : 170527598
Chosen Option : 4

Q.84 $\sqrt{(22+37-15) \div 11 \times 13} - 3 =$

- Ans
- ☐ 1. 11
 - ☐ 2. 3
 - ☐ 3. 13
 - ☒ 4. 7

Question ID : 170527581
Chosen Option : 4

Q.85 The sculptor who carved the Gunpark statue built as a symbol of the martyrs (369) of the 1969 Special Telangana Movement is

- Ans ☒ 1. B.S.Ramulu
☒ 2. Ekka Yadagi Rao
☒ 3. VVR Chari
☒ 4. Durgam Ravinder

Question ID : 170527593
Chosen Option : 4

Q.86 Choose the one which can be substituted for the given words/sentence.
"One who does not care for literature or art"

- Ans ☒ 1. Hypocrite
☒ 2. Dictator
☒ 3. Primitive
☒ 4. Philistine

Question ID : 170527591
Chosen Option : 1

Q.87 In a certain code language 'CODING is coded as 'DRIPWR then in the same language which word would be coded as 'YWUSQO'

- Ans ☒ 1. XTPLHD
☒ 2. DHLPTX
☒ 3. XTPMJE
☒ 4. YUQLHD

Question ID : 170527583
Chosen Option : 1

Q.88 In MS Word, macros are used for

- Ans ☒ 1. Editing Images using built-in VB code
☒ 2. Aggregating table rows or columns with given key combination
☒ 3. Automate the design of a document with a given key combination
☒ 4. Repeating a sequence of keystrokes with a given key combination

Question ID : 170527599
Chosen Option : 2

Q.89 The three new states of India that were created in 2000 are from

- Ans ☒ 1. Uttar Pradesh, Bihar and West Bengal
☒ 2. West Bengal, Uttar Pradesh and Maharashtra
☒ 3. Madhya Pradesh, Haryana and Rajasthan
☒ 4. Madhya Pradesh, Uttar Pradesh and Bihar

Question ID : 170527587
Chosen Option : 2

Q.90 Choose an appropriate ***preposition*** from the options:
What you say has hardly any bearing _____ the lives of tribes.

- Ans
- ☐ 1. for
 - ☐ 2. about
 - ☒ 3. on
 - ☐ 4. in

Question ID : 170527592
Chosen Option : 2

Q.91 Which is the correct formatting of a 'SUM' formula?

- Ans
- ☐ 1. SUMof(B1-B6)
 - ☐ 2. SUM (B1 to B6)
 - ☐ 3. =SUMOF(B1,B6)
 - ☒ 4. =SUM(B1:B6)

Question ID : 170527597
Chosen Option : 4

Q.92 The traditional art form of Telangana, which involves storytelling through puppetry, is called:

- Ans
- ☐ 1. Yakshagana
 - ☐ 2. Burrakatha
 - ☒ 3. Tholu Bommalata
 - ☐ 4. Kathakali

Question ID : 170527595
Chosen Option : 3

Q.93 Who is the renowned Telangana artist known for his pioneering work in the Cherial Scroll painting style?

- Ans
- ☐ 1. P. S. Ramakrishna
 - ☐ 2. Surya Prakash
 - ☒ 3. Thota Vaikuntam
 - ☐ 4. Laxma Goud

Question ID : 170527594
Chosen Option : 4

Q.94 Tsunamis are not caused by?

- Ans
- ☐ 1. Earthquakes
 - ☒ 2. Hurricanes
 - ☐ 3. Volcanic eruptions
 - ☐ 4. Undersea landslides

Question ID : 170527585
Chosen Option : 3

Q.95 Author and poet Mercy Margaret won the 2017 Sahitya Akademi Yuva Puraskar for the book

- Ans ☒ 1. Maata Muchata
☒ 2. Maatalu Muchatlu
☒ 3. Maatala Madugu
☒ 4. Maatala Mantalu

Question ID : 170527596
Chosen Option : 2

Q.96 The present chairman of the chiefs of staff committee in the Indian Armed Forces is

- Ans ☒ 1. Anil Chauhan
☒ 2. Birender Singh Dhanaa
☒ 3. Manoj Mukund Naravane
☒ 4. Bipin Rawat

Question ID : 170527586
Chosen Option : 4

Q.97 The salaries of three persons A, B and C are in the ratio 2 : 4 : 5. If the salaries of A, B and C are increased by 30%, 25% and 20% respectively, then the ratio of their new salaries in the same order is

- Ans ☒ 1. 3 : 5 : 5
☒ 2. 13 : 25 : 30
☒ 3. 12 : 20 : 25
☒ 4. 15 : 25 : 28

Question ID : 170527582
Chosen Option : 2

Q.98 How is a logo that appears in the same position on all the slides is added in Power Point?

- Ans ☒ 1. Insert logo on notes master
☒ 2.
There is no direct way. It must be inserted manually on each slide
☒ 3. Insert logo on the slide master
☒ 4. Insert logo on handout master

Question ID : 170527600
Chosen Option : 1

Q.99 The river that flows towards the west is

- Ans ☒ 1. Narmada
☒ 2. Cauvery
☒ 3. Krishna
☒ 4. Godavari

Question ID : 170527588
Chosen Option : 4

Q.100 The Antonym of "Notorious " is -----.

- Ans  1. Famous
-  2. Uninterested
-  3. Tarnished
-  4. Vigorous

Question ID : **170527590**
Chosen Option : **4**